Design code:

```
≣ P1.v
                         x ≡ basvs master.xdc
module Register_Mux #(parameter WIDTH=18,REG_IDENTIFIER=1,RSTTYPE="SYNC") (input [WIDTH-1:0] X,input CLK ,rst,EN,output [WIDTH-1:0] out);
reg [WIDTH-1:0] X_reg;
        if(rst) X_reg<=0;
        else if(EN) X reg<=X;
always@(posedge CLK) begin
    if(RSTTYPE=="SYNC")begin
if(EN) begin
            if(rst) X_reg<=0;
            else X_reg <=X;
assign out =(REG_IDENTIFIER)?X_reg:X;
endmodule
module DSP48A1_Project (A,B,D,C,CLK,CARRYIN,OPMODE,BCIN,RSTA,RSTB,RSTM,RSTP,RSTC,RSTD,RSTCARRYIN,RSTOPMODE,
CEA,CEB,CEM,CEP,CEC,CED,CECARRYIN,CEOPMODE,PCIN,BCOUT,PCOUT,P,M,CARRYOUT,CARRYOUTF);
parameter A0REG=0;
parameter A1REG=1;
parameter B0REG=0;
parameter B1REG=1;
parameter CREG=1;
parameter DREG=1;
parameter MREG=1:
parameter PREG=1;
parameter CARRYINREG=1;
parameter OPMODEREG=1;
parameter CARRYINSEL= "OPMODE5";
parameter B_INPUT ="DIRECT";
parameter RSTTYPE ="SYNC";
//input/output declaration
input [47:0] C,PCIN;
input [7:0] OPMODE;
input CLK, CARRYIN, RSTA, RSTB, RSTM, RSTP, RSTC, RSTD, RSTCARRYIN, RSTOPMODE,
CEA, CEB, CEM, CEP, CEC, CED, CECARRYIN, CEOPMODE;
output [17:0] BCOUT;
output [47:0] PCOUT,P;
output CARRYOUT, CARRYOUTF;
wire [17:0] A0_reg,A1_reg,B0_input,B0_reg,B1_input,B1_reg,D_reg,Pre_add_sub_out;
wire [47:0] C_reg,concat_out,X_out ,Z_out;
wire [48:0] Post_add_sub_out;
wire[35:0] M_reg,multiplier_out;
wire [7:0] OPMODE_reg;
wire CARRYIN reg,CYI,CYO;
assign B0_input =(B_INPUT=="DIRECT")?B:BCIN;
 Register_Mux #(18,DREG,RSTTYPE) D_register (D,CLK,RSTD,CED,D_reg);
Register_Mux #(18,B0REG,RSTTYPE) B0_register (B0_input,CLK,RSTB,CEB,B0_reg);
Register Mux #(18,A0REG,RSTTYPE) A0 register (A,CLK,RSTA,CEA,A0 reg);
Register Mux #(18,A1REG,RSTTYPE) A1 register (A0 reg,CLK,RSTA,CEA,A1 reg);
Register_Mux #(48,CREG,RSTTYPE) C_register (C,CLK,RSTC,CEC,C_reg);
 Register_Mux #(8,0PMODEREG,RSTTYPE) OPMODE_register (OPMODE,CLK,RSTOPMODE,CEOPMODE,OPMODE_reg);
assign CYI =(CARRYINSEL=="OPMODE5")?OPMODE_reg[5]:(CARRYINSEL=="CARRYIN")?CARRYIN:0;
 Register_Mux #(1,CARRYINREG,RSTTYPE) CARRYIN_register (CYI,CLK,RSTCARRYIN,CECARRYIN,CARRYIN_reg);
assign Pre_add_sub_out =(OPMODE_reg[6])?(D_reg-B0_reg):(D_reg+B0_reg);
assign B1 input =(OPMODE reg[4])?Pre add sub out:B0 reg;
Register_Mux #(18,B1REG,RSTTYPE) B1_register (B1_input,CLK,RSTB,CEB,B1_reg);
assign BCOUT = B1_reg;
 assign multiplier_out = A1_reg*B1_reg;
 assign concat_out ={D[11:0],A1_reg,B1_reg};
 Register_Mux #(36,MREG,RSTTYPE) M_register (multiplier_out,CLK,RSTM,CEM,M_reg);
assign M =~(~M_reg);
 assign X_out=(OPMODE_reg[1:0]==0)?0:(OPMODE_reg[1:0]==1)?M_reg:(OPMODE_reg[1:0]==2)?P:concat_out;
assign Z_out=(OPMODE_reg[3:2]==0)?0:(OPMODE_reg[3:2]==1)?PCIN:(OPMODE_reg[3:2]==2)?P:C_reg;
assign Post_add_sub_out =(OPMODE_reg[7])?(Z_out-(X_out+CARRYIN_reg)):(Z_out+X_out+CARRYIN_reg);
 assign CYO = Post_add_sub_out[48];
 Register_Mux #(1,CARRYOUTREG,RSTTYPE) CARRYOUT_register (CYO,CLK,RSTCARRYIN,CECARRYIN,CARRYOUT);
 assign CARRYOUTF =CARRYOUT:
 Register_Mux #(48,PREG,RSTTYPE) P_register (Post_add_sub_out[47:0],CLK,RSTP,CEP,P);
```

Tb code:

```
■ P1_tb.v


■ run_tb.do
① Workspace Trust
                                                                       ≣ basys_master.xdc
      module Project_tb ();
      reg CLK, CARRYIN, RSTA, RSTB, RSTM, RSTP, RSTC, RSTD, RSTCARRYIN, RSTOPMODE, CEA, CEB, CEM, CEP, CEC, CED, CECARRYIN, CEOPMODE;
      reg [17:0] A,B,D,BCIN;
       reg [47:0] C,PCIN;
      wire CARRYOUT, CARRYOUTF;
       wire [17:0] BCOUT;
      wire [47:0] PCOUT,P;
       DSP48A1_Project DUT (A,B,D,C,CLK,CARRYIN,OPMODE,BCIN,RSTA,RSTB,RSTM,RSTP,RSTC,RSTD,RSTCARRYIN,RSTOPMODE,
       CEA,CEB,CEM,CEP,CEC,CED,CECARRYIN,CEOPMODE,PCIN,BCOUT,PCOUT,P,M,CARRYOUT,CARRYOUTF);
           CEA=1;CEB=1;CEM=1;CEP=1;CEC=1;CED=1;CECARRYIN=1;CEOPMODE=1;
           RSTA=1;RSTB=1;RSTM=1;RSTP=1;RSTC=1;RSTD=1;RSTCARRYIN=1;RSTOPMODE=1;
               $display("output is wrong");
               $stop;
           RSTA=0; RSTB=0; RSTP=0; RSTC=0; RSTD=0; RSTCARRYIN=0; RSTOPMODE=0; \\
           OPMODE='b00111101; //c+[([D+B].A)+OPMODE[5]]
D=1000;B=2000;A=3;C=10; //Expected output = 3311
               $display("output is wrong");
               $stop;
           OPMODE='b01011101; //C+[(D-B).A]
           D=35;B=15;A=5;C=50;//Expected output =150
               $display("output is wrong");
               $stop;
           OPMODE='b11001101; //C-(A.B)
               $display("output is wrong");
```

Do file:


```
≡ P1.v
                                ≣ P1 tb.v ● ≣ run tb.do X
1 vlib work
   vlog P1.v P1_tb.v
   vsim -voptargs=+acc work.Project_tb
   add wave
   add wave -position insertpoint \
   sim:/Project_tb/DUT/A0_reg \
   sim:/Project_tb/DUT/A1_reg \
   sim:/Project_tb/DUT/B0_reg \
   sim:/Project_tb/DUT/B1_reg \
  sim:/Project_tb/DUT/D_reg \
   sim:/Project_tb/DUT/C_reg \
   sim:/Project_tb/DUT/M_reg \
   sim:/Project_tb/DUT/OPMODE_reg \
   sim:/Project_tb/DUT/CARRYIN_reg
   run -all
   #quit -sim
```

Constrain file:


Test cases:

 


Elaborated design:

 


Synthesized design:

 

Implemented design:

 

Messages:

 

Utilization and timing reports:

